

Important questions for BEEE MID II

Short Questions

Short Questions	
1	What is the primary purpose of using a Zener diode in a circuit?
2	Draw the Forward bias and reverse bias diode characteristics
3	Describe the evolution of electronics
4	List the three configurations of a Bipolar Junction Transistor (BJT).
5	What is the use of Amplifier.
6	Draw the block diagram of a DC power supply.
7	Draw the block diagram of an electronic instrumentation system
8	What is the frequency response of a common emitter (RC coupled) amplifier?
9	What is the function of a capacitor filter in a rectifier circuit?
10	Define the functionality of a NOT gate.
11	Where do you apply logic gates?
12	What are the universal gates?
13	What is the purpose of using Excess-3 code in digital systems?
14	What is a flip- flop in digital electronics?
15	Write the truth-table for AND gate.

Long Questions:

Long Questions	
1	Discuss about the operation of PN junction diode both in Forward bias and Reverse bias conditions with suitable diagrams.
2	Write the differences between N Type and P Type Material.
3	Explain about working of BJT Transistor.
4	Describe and draw the Characteristics of Zener Diode.
5	Discuss on semiconductor devices and evaluations of electronics?
6	Differentiate between BJT CB, CE, CC Configurations.
7	Describe the block diagram of Public Address system.
8	Explain in detail about common emitter (RC coupled) amplifier.
9	Explain the working of a full wave bridge rectifier.
10	Provide a neat block diagram description of a DC power supply?
11	Explain the working of simple Zener voltage regulator.
12	Discuss about the block diagram of an electronic instrumentation system.
13	Write truth tables of gates AND, OR, NOR, NAND?
14	What are the universal gates and Implement a XOR gate logic function using only NAND gates.
15	Discuss in detail about Half adder and Full adder.
16	Explain in detail about Excess-3 code.
17	Discuss in detail about Flip flops.
18	Explain in detail about Registers and counters.